

9. 4 bit ripple carry adder.

Each full Adder is implemented using a 3 input xor gate, 3 2 input AND gate and one 3 input OR gate.



3 input xor gate delay = 3 nsec.

2 input And gate = 1 nsec.

3 input or gate = 1 nsec.

Total time taken to perform addition?

Ans.

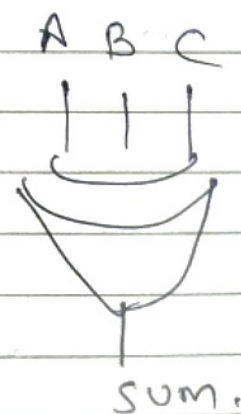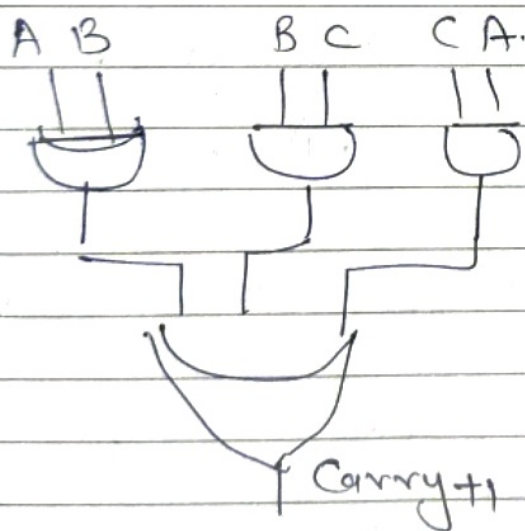

for one full Adder, Prop. time

$$= \max.(\text{xorgate}, \text{AND}, \text{OR})$$

$$= \max(3, 1, 1) = 3 \text{ nsec.}$$

Total prop. time for 4 full Adder

$$= 4 \times 3 = 12 \text{ nsec.}$$

Q. 4 bit ripple carry adder.


Prop. time = X OR 20 ns
AND 15 ns
OR 10 ns.

time taken for Carry out at 4th f.A.

time taken for Sum perform.

Ans.

At 4th f.A.

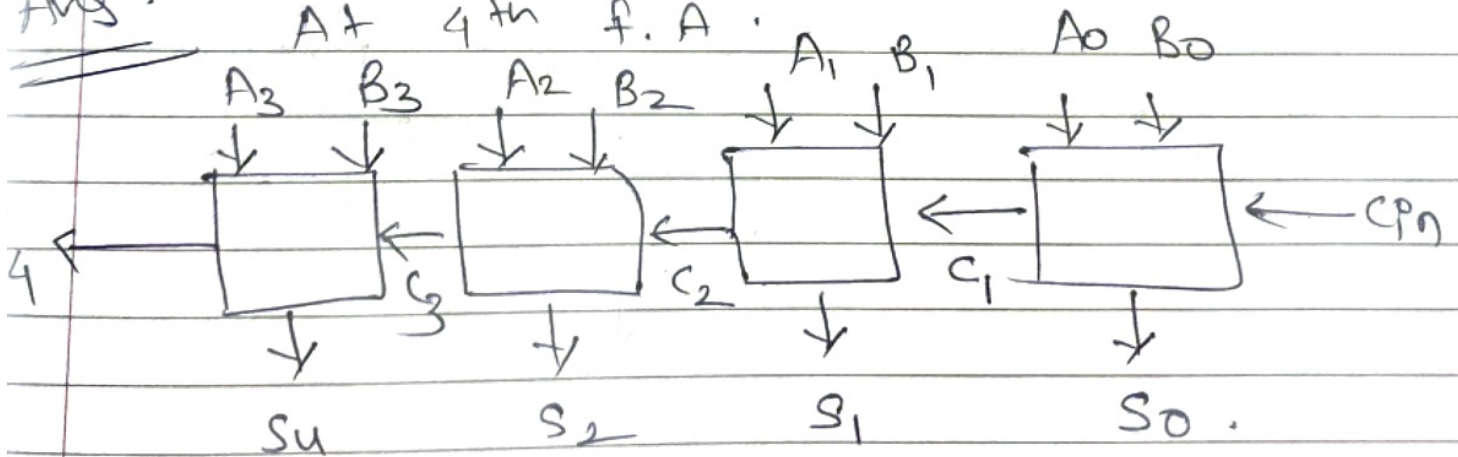

$$\text{Carry-4} \Rightarrow 4 \times \text{Carry time.}$$

$$\text{Carry time} = \text{Xor} + \text{And} + \text{or.}$$

$$= 20 + 15 + 10 = 45 \text{ nsec.}$$

$$\text{Carry 4} = 4 \times 45.$$

$$\text{Sum 4} = 3 \times \text{Carry time} + \text{S4 time}$$

$$= 3 \times 45 + (20 + 20) \checkmark$$

$$= 40 + 135 \checkmark$$


| | $\overline{A}B$ | $\overline{A}\overline{B}$ | AB | $A\overline{B}$ |
|----------------------------|-----------------|----------------------------|------|-----------------|
| $\overline{C}D$ | | * 1 | 1 | |
| $\overline{C}\overline{D}$ | 1 | 1 | 1 | |
| CD | 1 | | * 1 | 1 |
| $C\overline{D}$ | | | 1 | 1 |

$\epsilon PI = 2$

① CA


② $\overline{C}B$

Prime Imp $\rightarrow 6$ ✓

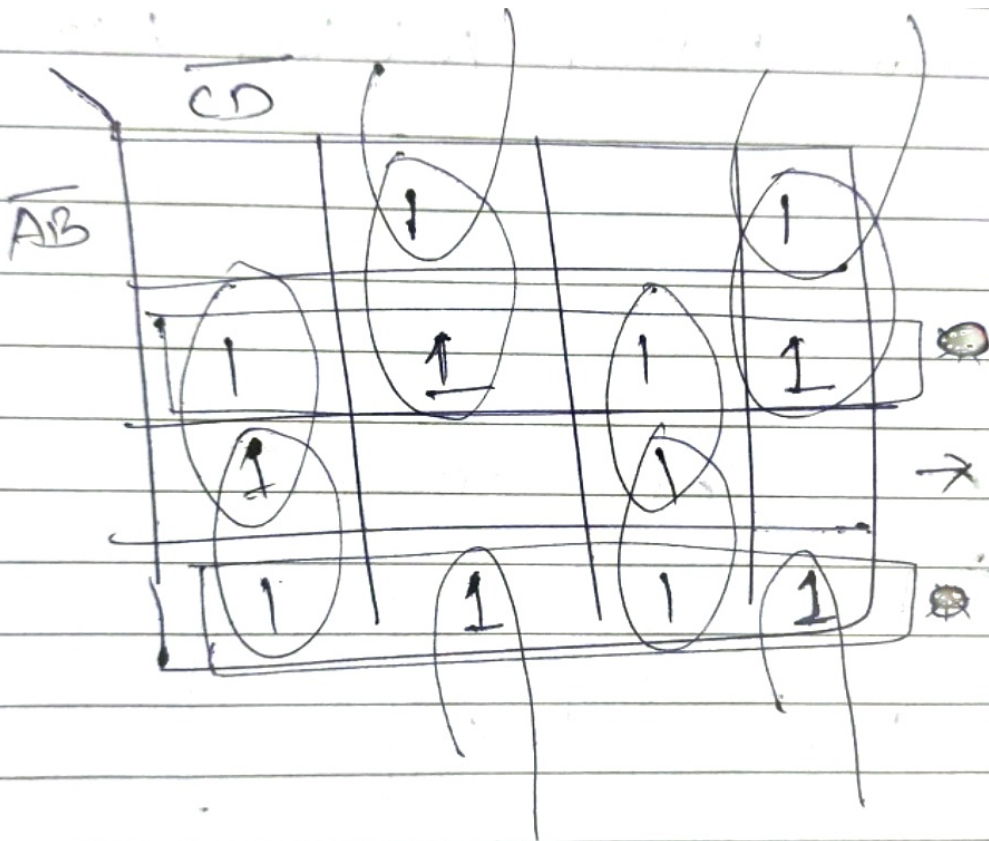

→ NO. EPI.

Prime Imp →

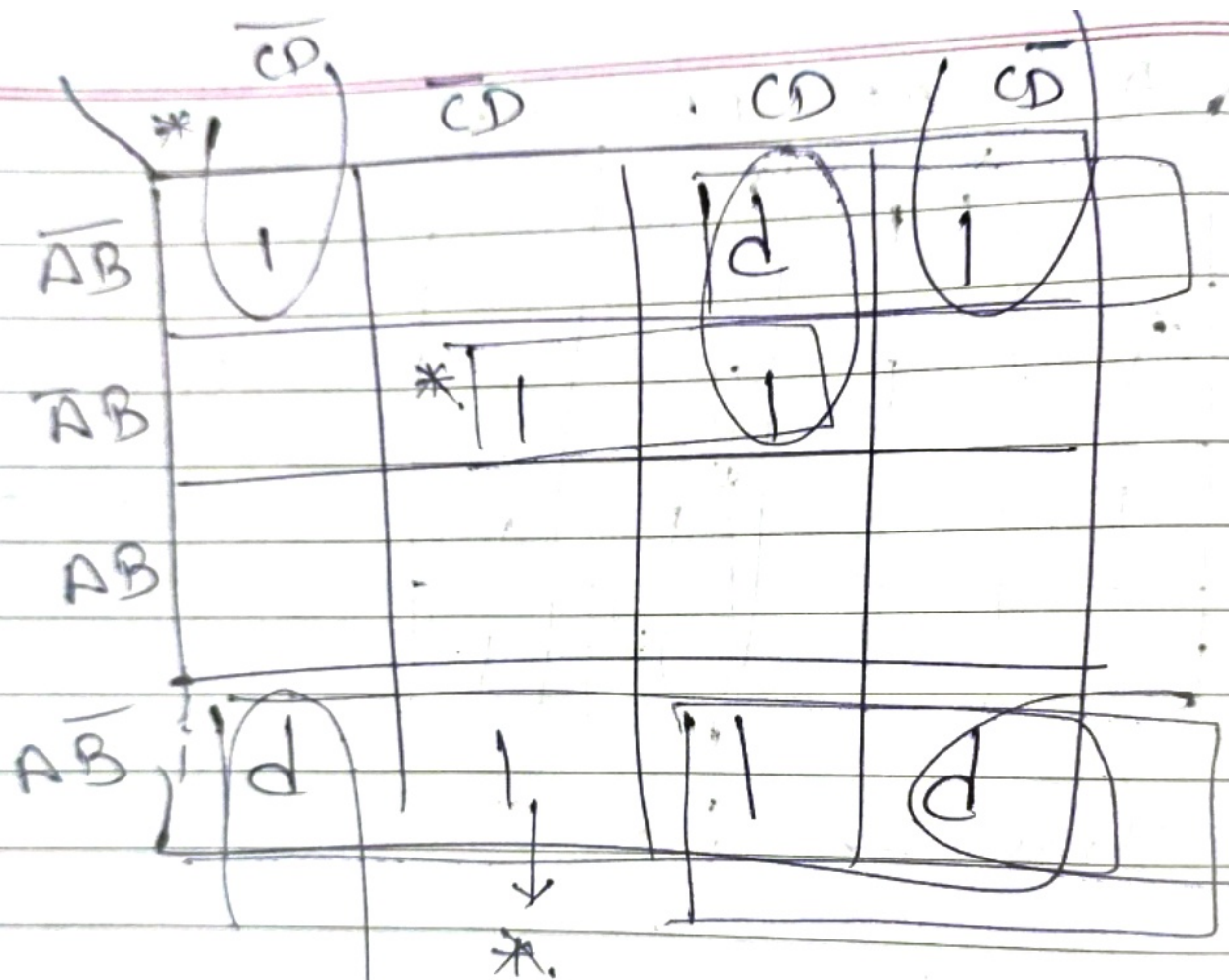


EPI $\rightarrow \overline{B}\overline{D}, A'\overline{B}D, A\overline{B}$.

| | $\bar{C}\bar{D}$ | $\bar{C}D$ | CD | $C\bar{D}$ |
|------------------|------------------|------------|------|------------|
| $\bar{A}\bar{B}$ | *1 | | | |
| $\bar{A}B$ | 1 | 1 | X | |
| AB | | X | 1 | 1 |
| $A\bar{B}$ | | | | 1* |


2 EPI $\rightarrow \bar{A}\bar{C}\bar{D}, A\bar{C}\bar{D}$.

$$PI = 5.$$

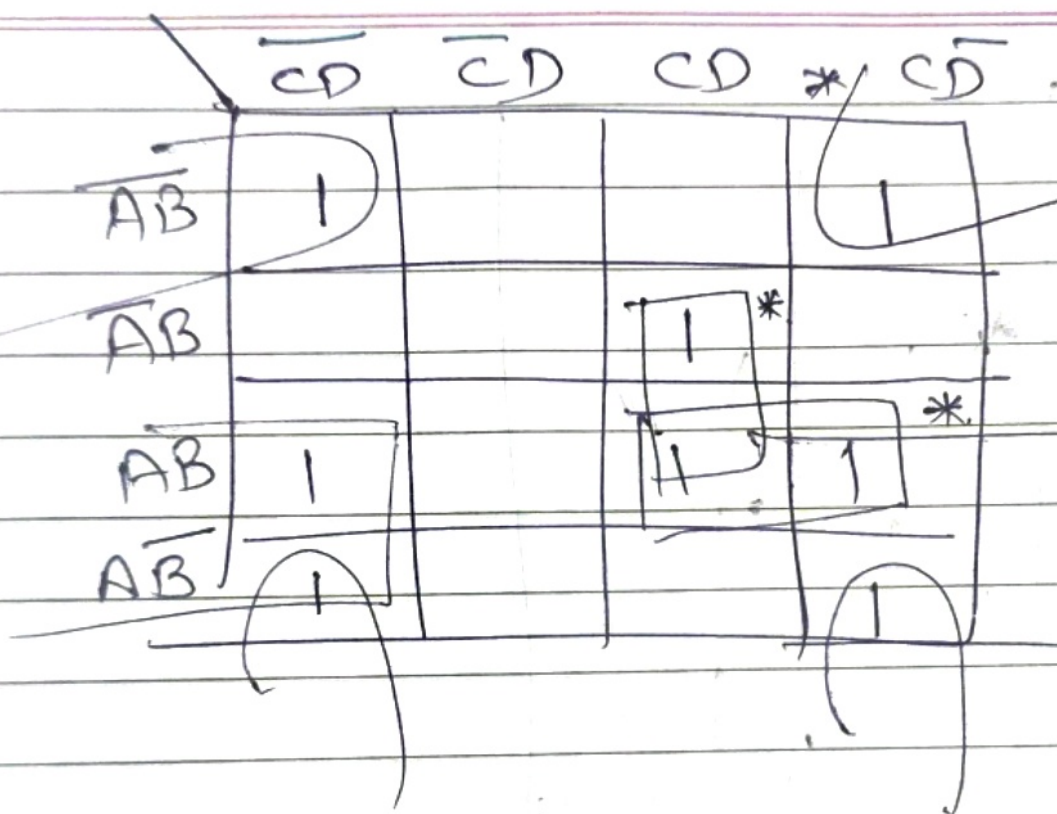

3 EPI — $\overline{B}\overline{D}$, $A\overline{D}$, BCD ✓

PI → 4.

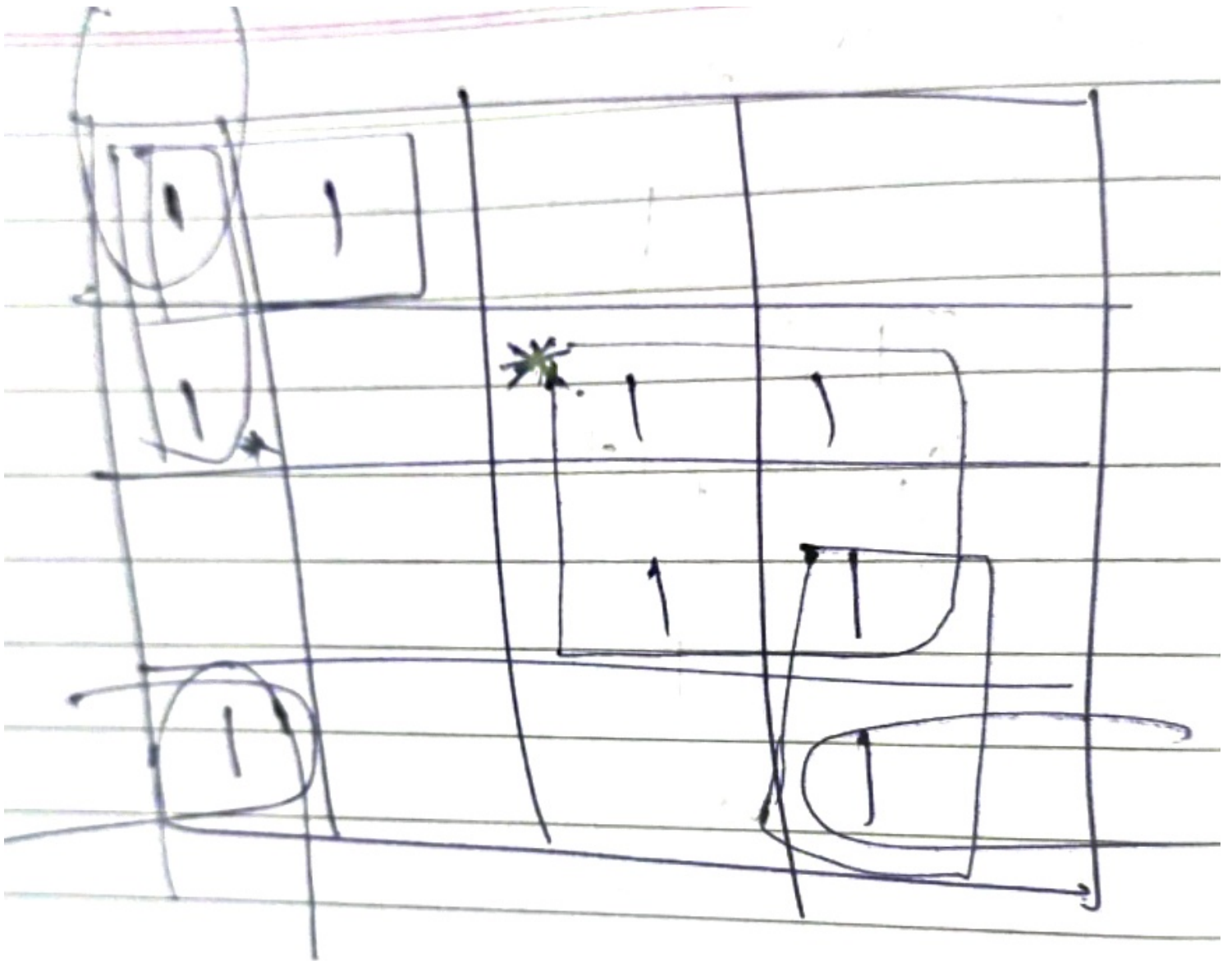

EP I → 2 . . .

PI →